

 [PetrDockalik](#) / [Digital-electronics-1](#)

 MIT License

☆ 0 stars 🍴 0 forks

☆ Star



👁 Unwatch ▼

- Code
- Issues
- Pull requests
- Actions
- Projects
- Wiki
- Security
- Insights
- Settings

🔗 main ▼




...

[Digital-electronics-1](#) / [Labs](#) / [06-display_driver](#) / [README.md](#)

 **PetrDockalik** [LAB6] Complete 

👤 1 contributor

RawBlame

323 lines (264 sloc) | 9.58 KB




Laboratory 6 - Display driver

More information on [GitHub Tomáš Frýza](#)

[My GitHub](#)

Preparation of Laboratory

[WaveDrom](#)

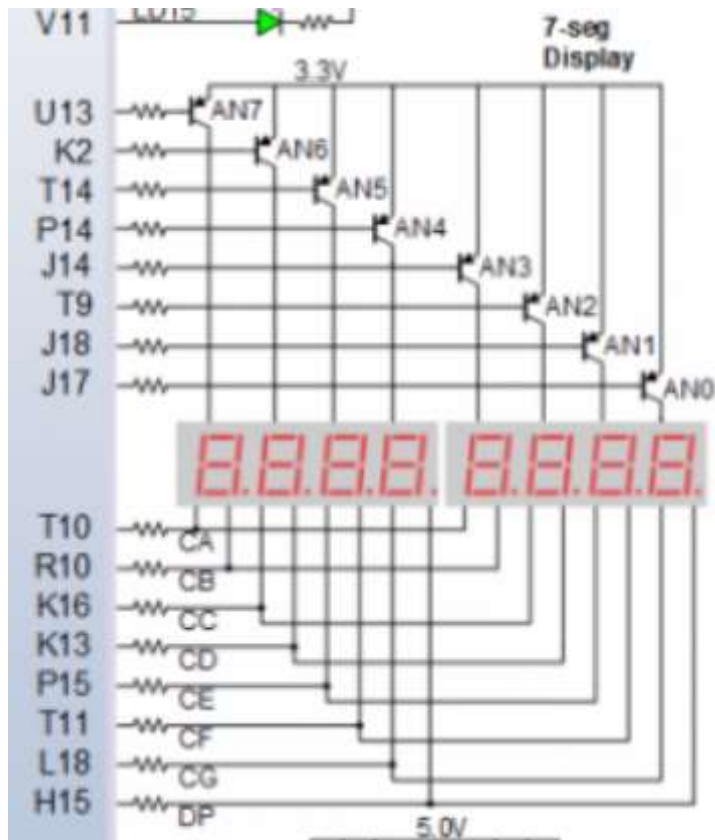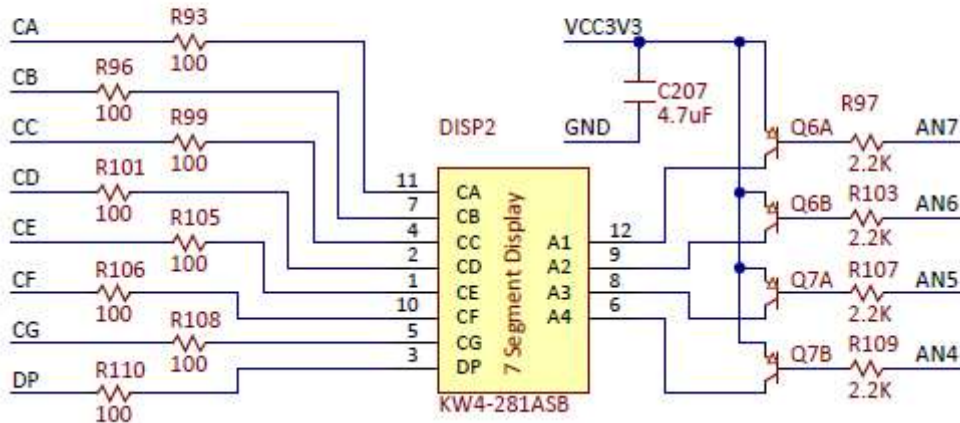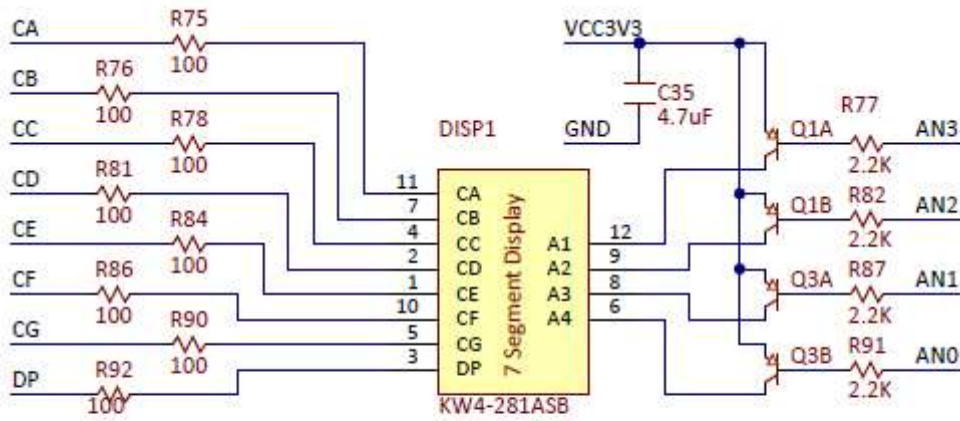


```
{
  signal:
  [
    ['Digit position',
      {name: 'Common anode: AN(3)', wave: 'xx01..01..01'},
      {name: 'AN(2)', wave: 'xx101..01..0'}],
  ]
}
```

```

    {name: 'AN(1)', wave: 'xx1.01..01..'},
    {name: 'AN(0)', wave: 'xx1..01..01..'},
  ],
  ['Seven-segment data',
    {name: '4-digit on display', wave: 'xx3333555599', data: ['3','1','4','2','3','1','4','2','3','1'],
    {name: 'Cathods A: CA', wave: 'xx01.0.1.0.1'},
    {name: 'CB', wave: 'xx0.....'},
    {name: 'CC', wave: 'xx0..10..10..'},
    {name: 'CD', wave: 'xx01.0.1.0.1'},
    {name: 'CE', wave: 'xx1..01..01..'},
    {name: 'CF', wave: 'xx1.01..01..'},
    {name: 'CG', wave: 'xx010..10..1'},
  ],
  {name: 'Decimal point: DP', wave: 'xx01..01..01'},
],
head:
{
  text: '
    4ms 4ms 4ms 4ms 4ms 4ms 4ms 4ms 4ms 4ms
},
}

```

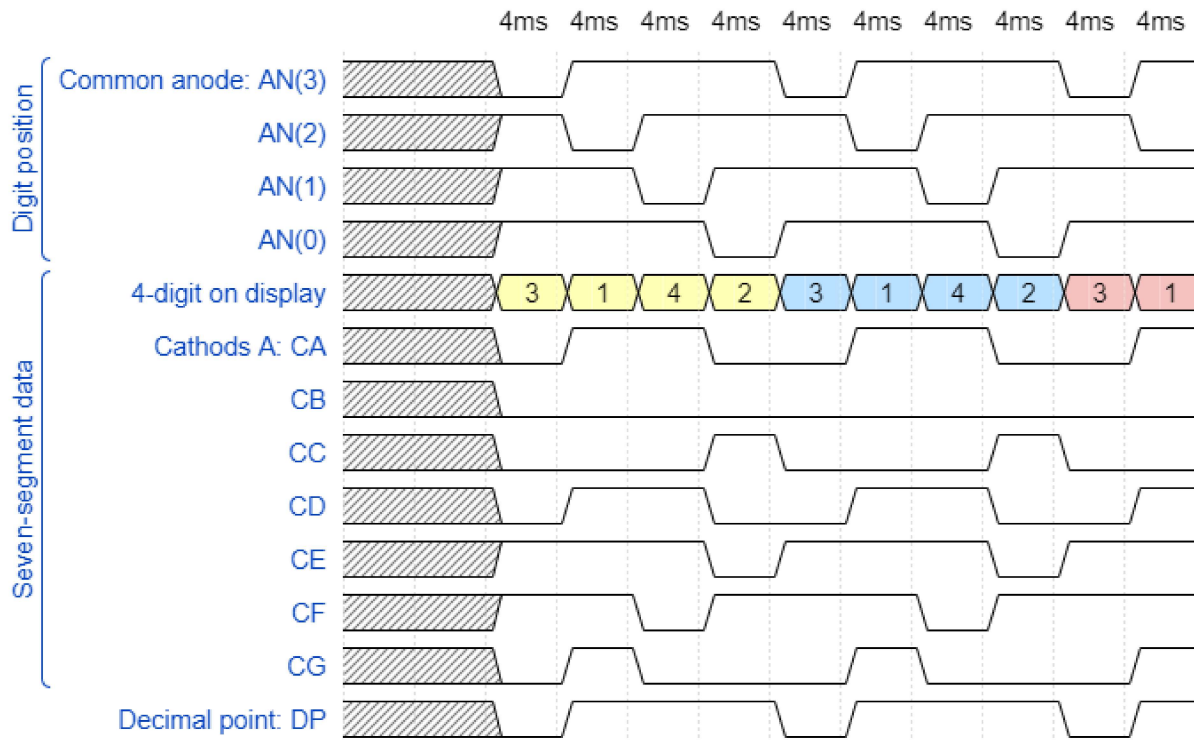

Laboratory

Driver.vhd

```

p_mux : process(s_cnt, data0_i, data1_i, data2_i, data3_i, dp_i)
begin
  case s_cnt is
    when "11" =>

```

```

        s_hex <= data3_i;
        dp_o  <= dp_i(3);
        dig_o <= "0111";

    when "10" =>
        s_hex <= data2_i;
        dp_o  <= dp_i(2);
        dig_o <= "1011";

    when "01" =>
        s_hex <= data1_i;
        dp_o  <= dp_i(1);
        dig_o <= "1101";

    when others =>
        s_hex <= data0_i;
        dp_o  <= dp_i(0);
        dig_o <= "1110";
    end case;
end process p_mux;

```

Testbench_driver.vhd

```

-----
--
-- Template for 4-digit 7-segment display driver testbench.
-- Nexys A7-50T, Vivado v2020.1.1, EDA Playground
--
-- Copyright (c) 2020-Present Tomas Fryza
-- Dept. of Radio Electronics, Brno University of Technology, Czechia
-- This work is licensed under the terms of the MIT license.
--
-----

library ieee;
use ieee.std_logic_1164.all;

-----
-- Entity declaration for testbench
-----
entity tb_driver_7seg_4digits is
    -- Entity of testbench is always empty
end entity tb_driver_7seg_4digits;

-----
-- Architecture body for testbench
-----
architecture testbench of tb_driver_7seg_4digits is

    -- Local constants
    constant c_CLK_100MHZ_PERIOD : time    := 10 ns;

```

```

--Local signals
signal s_clk_100MHz : std_logic;
signal s_reset      : std_logic;
signal s_data0_i    : std_logic_vector(4 - 1 downto 0);
signal s_data1_i    : std_logic_vector(4 - 1 downto 0);
signal s_data2_i    : std_logic_vector(4 - 1 downto 0);
signal s_data3_i    : std_logic_vector(4 - 1 downto 0);
signal s_dp_i       : std_logic_vector(4 - 1 downto 0);
signal s_dp_o       : std_logic;
signal s_seg_o      : std_logic_vector(7 - 1 downto 0);
signal s_dig_o      : std_logic_vector(4 - 1 downto 0);

begin
-- Connecting testbench signals with driver_7seg_4digits entity
-- (Unit Under Test)
uut_cnt : entity work.driver_7seg_4digits
    port map(
        clk      => s_clk_100MHz,
        reset    => s_reset,
        data0_i  => s_data0_i,
        data1_i  => s_data1_i,
        data2_i  => s_data2_i,
        data3_i  => s_data3_i,
        dp_i     => s_dp_i,
        dp_o     => s_dp_o,
        seg_o    => s_seg_o,
        dig_o    => s_dig_o
    );

-----
-- Clock generation process
-----
p_clk_gen : process
begin
    while now < 750 ms loop          -- 75 periods of 100MHz clock
        s_clk_100MHz <= '0';
        wait for c_CLK_100MHZ_PERIOD / 2;
        s_clk_100MHz <= '1';
        wait for c_CLK_100MHZ_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

-----
-- Reset generation process
-----
p_reset_gen : process
begin
    s_reset <= '0';
    wait for 150 ms;

    -- Reset activated
    s_reset <= '1';
    wait for 50 ms;

```

```
s_reset <= '0';
wait for 100 ms;

s_reset <= '1';
wait for 35 ms;

s_reset <= '0';
wait;
end process p_reset_gen;

-----
-- Data generation process
-----
p_stimulus : process
begin
    report "Stimulus process started" severity note;

    s_dp_i <= "0111";
    s_data0_i <= "0010";

    s_data1_i <= "0100";

    s_data2_i <= "0001";



    s_data3_i <= "0011";

    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;


end architecture testbench;
```

Simulace


Průběhy vypadají stejné.

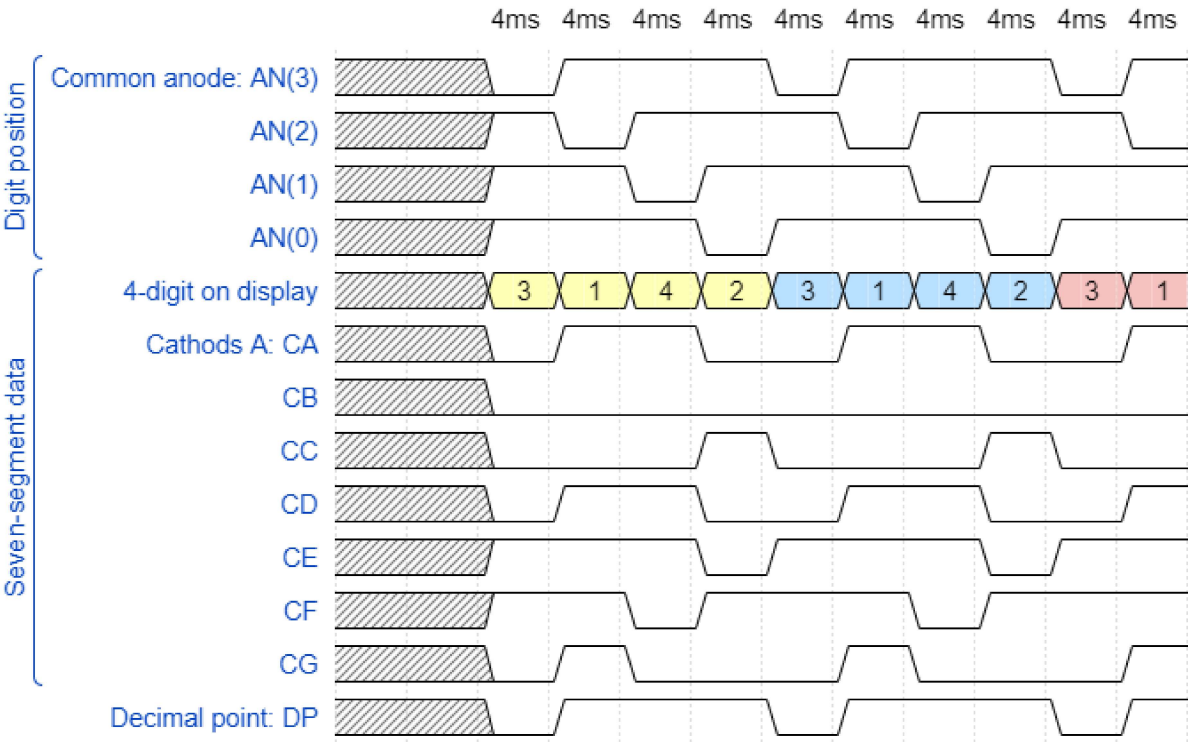 

Simulace před resetem

 


Simulace po resetu

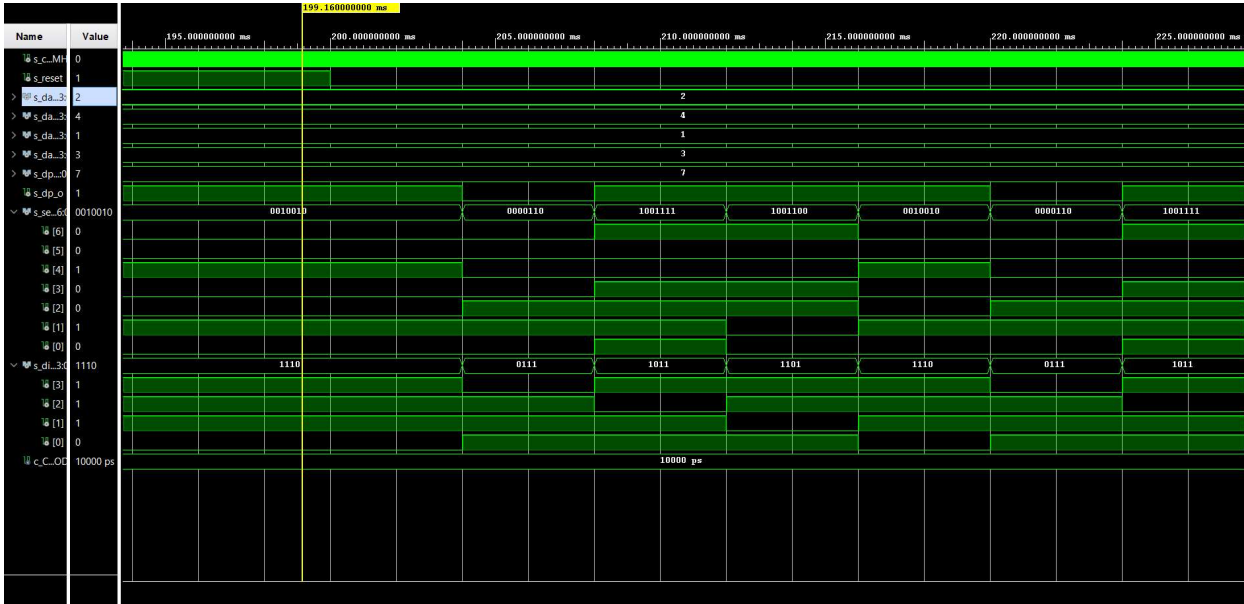

Simulace clock_enable 4ms

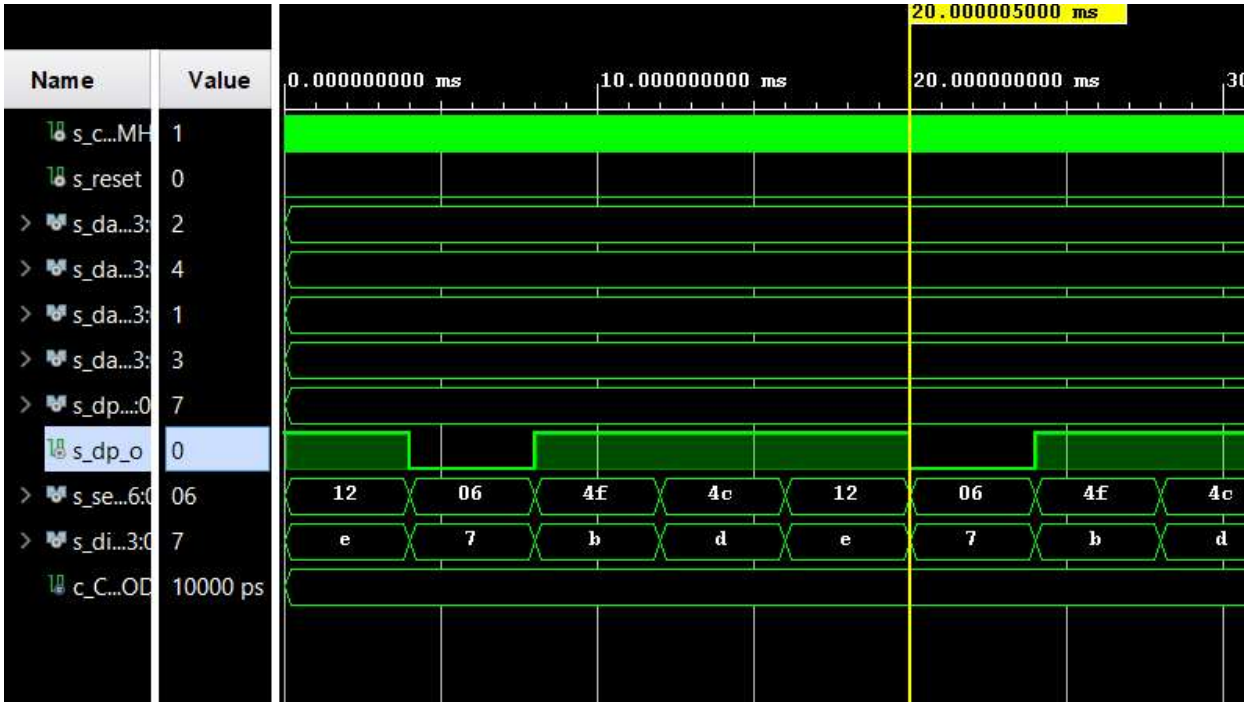Jasně vidíme, že do 20ms se nám displej 5x změnil.



Top.vhd

```
-----
-- Company:
-- Engineer:
--
-- Create Date: 22.03.2021 15:55:36
-- Design Name:
-- Module Name: top - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

```

entity top is
    Port ( CLK100MHZ : in STD_LOGIC;           -- Main clock
          BTNC : in STD_LOGIC;                 -- Synchronous reset
          SW : in STD_LOGIC_VECTOR (16-1 downto 0); -- Four 4-bit values
          CA : out STD_LOGIC;                  -- Cathod A
          CB : out STD_LOGIC;                  -- Cathod B
          CC : out STD_LOGIC;                  -- Cathod C
          CD : out STD_LOGIC;                  -- Cathod D
          CE : out STD_LOGIC;                  -- Cathod E
          CF : out STD_LOGIC;                  -- Cathod F
          CG : out STD_LOGIC;                  -- Cathod G
          DP : out STD_LOGIC;                  -- Decimal point
          AN : out STD_LOGIC_VECTOR (8-1 downto 0)); -- Common anode signals  tc
end top;

-----
-- Architecture body for top level
-----

architecture Behavioral of top is
    -- No internal signals
begin

    -----
    -- Instance (copy) of driver_7seg_4digits entity
    driver_seg_4 : entity work.driver_7seg_4digits
        port map(
            clk          => CLK100MHZ,
            reset        => BTNC,
            data3_i(3)   => SW(15),
            data3_i(2)   => SW(14),
            data3_i(1)   => SW(13),
            data3_i(0)   => SW(12),
            data2_i(3)   => SW(11),
            data2_i(2)   => SW(10),
            data2_i(1)   => SW(9),
            data2_i(0)   => SW(8),
            data1_i(3)   => SW(7),
            data1_i(2)   => SW(6),
            data1_i(1)   => SW(5),
            data1_i(0)   => SW(4),
            data0_i(3)   => SW(3),
            data0_i(2)   => SW(2),
            data0_i(1)   => SW(1),
            data0_i(0)   => SW(0),
            dp_i         => "0111",
            dp_o         => DP,
            seg_o(6)     => CA,
            seg_o(5)     => CB,
            seg_o(4)     => CC,
            seg_o(3)     => CD,
            seg_o(2)     => CE,
            seg_o(1)     => CF,
            seg_o(0)     => CG,
            dig_o(3)     => AN(3),

```

```

    dig_o(2) => AN(2),
    dig_o(1) => AN(1),
    dig_o(0) => AN(0)
  );

  -- Disconnect the top four digits of the 7-segment display
  AN(7 downto 4) <= b"1111";

end architecture Behavioral;

```

8-digit driver

Raději jsem zvolil clock_enable 2ms, protože při 4ms by to už mohlo jít poznat.

